

## Laplace Transform

- What it does?

Laplace transform converts the time domain signal to frequency domain signal.

Time domain signal  $\rightarrow$  frequency domain signal.

$$f(t) \rightarrow f(s).$$

$$\mathcal{L}[f(t)] \rightarrow F(s) = \int_{0^-}^{\infty} f(t) e^{-st} dt.$$

\*  $0^-$  is mandatory because for delta signal or impulse signal  $0^-$  required.

Here  $s = \sigma + j\omega$ .

Table of Laplace Transform pairs.

	$f(t)$	$F(s)$
1	$u(t)$	$1/s$
2	$t$	$1/s^2$
3	$e^{at}$	$\frac{1}{s-a}$
4	$e^{-at}$	$\frac{1}{s+a}$
5	$\delta(t)$	$1$
6	$K$	$K/s$
7	$\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$
8	$\cos \omega t$	$s / (s^2 + \omega^2)$

$$\begin{aligned} \mathcal{L}[u(t)] &= \int_{0^-}^{\infty} u(t) e^{-st} dt & \left| \begin{array}{l} u(t) = 1 \quad t > 0 \\ = 0 \quad t < 0 \end{array} \right. \\ &= \int_{0^-}^{\infty} e^{-st} dt \\ &= \left[ \frac{e^{-st}}{-s} \right]_0^{\infty} \\ &= -\frac{1}{s} [0 - 1] = \frac{1}{s} \end{aligned}$$

Important properties of Laplace Transform.

1) Linearity  $\mathcal{L}[a f_1(t) + b f_2(t)]$   
 $= a f_1(s) + b f_2(s)$


2) Time Differentiation

$$\mathcal{L}\left[\frac{d}{dt} f(t)\right] = s f(s) - f(0^-)$$

3) Time Integration

$$\mathcal{L}\left[\int_0^t f(t) dt\right] = \frac{1}{s} f(s)$$
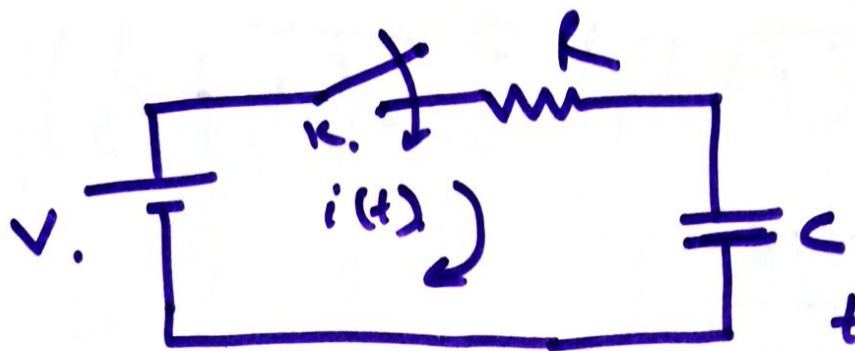
# Analysis of R-C. Series circuit using Laplace Transform



When switch is closed, at  $t=0$ .

By K.V.L

$$V u(t) = iR + \frac{1}{C} \int_{-\infty}^t i dt.$$

By L.T

$$\frac{V}{s} = I(s)R + \frac{1}{C} \left[ \frac{I(s)}{s} + \frac{q(0^-)}{s} \right]$$

By Applying Propy. T.I.

$\frac{q(0^-)}{s} =$  If there was initial voltage.

A  $\frac{q}{C} =$  voltage

But there  $\rightarrow$  no initial voltage

so,

$$q(0^-) = 0.$$

~~$$\frac{V}{s} = I(s)R + \frac{1}{Cs}$$~~

$$\frac{V}{s} = R I(s) + \frac{1}{Cs} I(s)$$

$$= I(s) \left[ R + \frac{1}{sC} \right]$$

$$I(s) = \frac{V}{s \left( R + \frac{1}{sC} \right)} = \frac{V/R}{s \left[ 1 + \frac{1}{RCs} \right]}$$

$$I(s) = \frac{V/R}{s + \frac{1}{RC}}$$

By Applying Inverse L.T.


$$i(t) = \frac{V}{R} \left( \frac{1}{s + \frac{1}{RC}} \right) \quad \left| \begin{array}{l} \frac{1}{s + \frac{1}{RC}} \text{ is} \\ \text{the form of} \\ \frac{1}{s+a} \end{array} \right.$$

$$\boxed{i(t) = \frac{V}{R} e^{-\frac{t}{RC}}}$$

### Analysis of R-L Circuit

If an impulse voltage is applied

$V(t)$  then

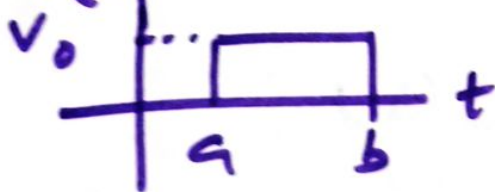

$$V(t) = V_0 [u_a(t) - u_b(t)]$$

then

$$I(s) = \frac{V}{R} \left[ u_a(t) e^{-\frac{1}{RC}(t-a)} - u_b(t) e^{-\frac{1}{RC}(t-b)} \right]$$