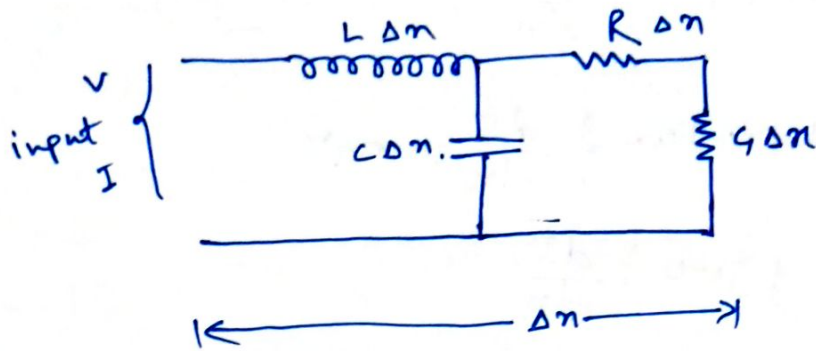


Transmission line equations & solutions



For small length Δx

The inductance will be $L\Delta x$
 capacitance " $C\Delta x$.
 Resistance " $R\Delta x$.
 Admittance " $G\Delta x$.

$$\Delta V = \cancel{R\Delta x} - (R\Delta x + j\omega L\Delta x) \cdot I$$

-ve sign indicates that at output there will be less value than the input value.

So

$$\lim_{\Delta x \rightarrow 0} \frac{\Delta V}{\Delta x} = \cancel{R} - (R + j\omega L) I$$

$$\frac{dv}{dx} = -(R + j\omega L) I \quad \text{--- (1)}$$

In the same manner

$$\Delta I = -(G\Delta x + j\omega C) V$$

Here -ve sign indicate that at output terminal there will be less current than the input

$$\lim_{\Delta x \rightarrow 0} \frac{\Delta I}{\Delta x} = -(G + j\omega C) V$$

$$\text{or, } \frac{dI}{dx} = -(G + j\omega C) V \quad \text{--- (2)}$$

After differentiating eqⁿ (1) again

$$\frac{d^2 v}{dn^2} = -(R + j\omega L) \frac{dI}{dn}$$

Putting the value of $\frac{dI}{dn}$ in eqⁿ

$$\frac{d^2 v}{dn^2} = -(R + j\omega L) \frac{dI}{dn}$$

$$\frac{d^2 v}{dn^2} = -(R + j\omega L) \times -(G + j\omega C) v$$
$$= (R + j\omega L)(G + j\omega C) \cdot v$$

$$\frac{d^2 v}{dn^2} = \gamma^2 \cdot v$$

$$\text{Here } \gamma^2 = (R + j\omega L) \times$$

$$\gamma^2 = (R + j\omega L)(G + j\omega C)$$

If we solve the above eqⁿ in space & time terms.

$$v(n, t) = v^+ e^{-\gamma n} + v^- e^{+\gamma n}$$

for instantaneous value of voltage.

$$v(n, t) = (v^+ e^{-\gamma n} + v^- e^{+\gamma n}) e^{j\omega t}$$

γ = Propagation constant.

$$\text{Also } \gamma = \alpha + j\beta$$

α = attenuation constant.

β = phase constant.

for lossless medium

$$\alpha = 0$$

$$V(z, t) = V^+ e^{-(\alpha + j\beta)z} e^{j\omega t} + V^- e^{+(\alpha + j\beta)z} e^{j\omega t}$$

$$= V^+ e^{-j\beta z} e^{j\omega t} + V^- e^{-j\beta z} e^{-j\omega t}$$

$$= V^+ e^{j(\omega t - \beta z)} + V^- e^{j(\omega t + \beta z)}$$

$$= V^+ \cos(\omega t - \beta z) + V^- \cos(\omega t + \beta z) \quad \text{--- (A)}$$

$$\therefore E = E_0 e^{-\alpha z} \cos(\omega t - \beta z) \hat{n}$$

$$E = E_0 \cos(\omega t - \beta z) \hat{n} \quad (\text{lossless medium}) \quad \text{--- (A)}$$

Comparing the eq. (B) & A we can conclude that the voltage travelling in transmission line like a wave.

$$V^+ \cos(\omega t - \beta z) \longrightarrow \text{in } +z \text{ direction}$$

$$V^- \cos(\omega t + \beta z) \longrightarrow \text{in backward direction.}$$

$$\frac{dv}{dz}$$